

DC and AC analysis - Differential amplifier

The circuit is shown in figure, v_1 and v_2 are the two inputs, applied to the bases of Q_1 and Q_2 transistors. The output voltage is measured between the two collectors C_1 and C_2 , which are at same dc potentials.

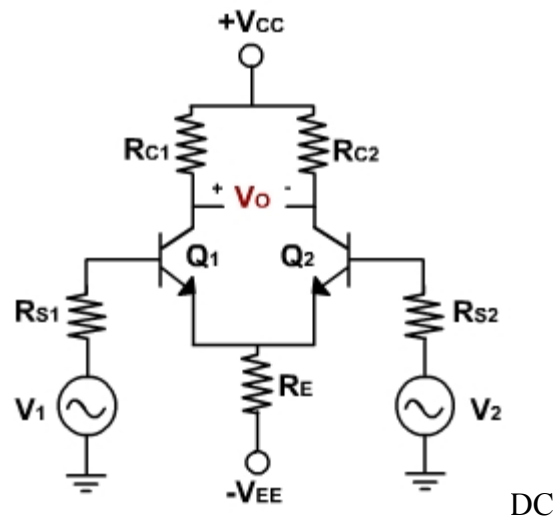


Figure 1.6

A.C. Analysis: In previous lecture dc analysis has been done to obtain the operating point of the two transistors. To find the voltage gain A_d and the input resistance R_i of the differential amplifier, the ac equivalent circuit is drawn using r-parameters as shown in [fig. 2](#). The dc voltages are reduced to zero and the ac equivalent of CE configuration is used.

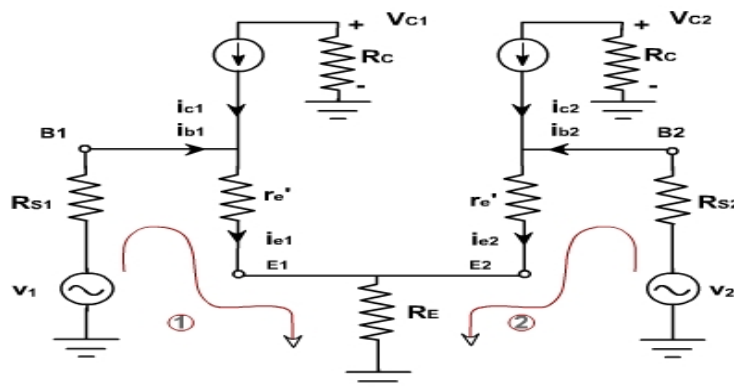


Figure 1.7

Since the two dc emitter currents are equal. Therefore, resistance r'_{e1} and r'_{e2} are also equal and designated by r'_e . This voltage across each collector resistance is shown 180° out of phase with respect to the input voltages v_1 and v_2 . This is same as in CE configuration. The polarity of the output voltage is shown in Figure. The collector C_2 is assumed to be more positive with respect to collector C_1 even though both are negative with respect to ground.

Applying KVL in two loops 1 & 2.

$$\begin{aligned} v_1 &= R_{s1} i_{b1} + i_{e1} r'_e + (i_{e1} + i_{e2}) R_E \\ v_2 &= R_{s2} i_{b2} + i_{e2} r'_e + (i_{e1} + i_{e2}) R_E \end{aligned}$$

Substituting current relations,

$$\begin{aligned} i_{b1} &= \frac{i_{e1}}{\beta}, \quad i_{b2} = \frac{i_{e2}}{\beta} \\ V_1 &= \frac{R_{s1}}{\beta} i_{e1} + r'_e i_{e1} + R_E (i_{e1} + i_{e2}) \\ V_2 &= \frac{R_{s2}}{\beta} i_{e2} + r'_e i_{e2} + R_E (i_{e1} + i_{e2}) \end{aligned}$$

Again, assuming R_{s1}/β and R_{s2}/β are very small in comparison with R_E and r'_e and therefore neglecting these terms,

$$\begin{aligned} (r'_e + R_E) i_{e1} + R_E i_{e2} &= v_1 \\ R_E i_{e1} + (r'_e + R_E) i_{e2} &= v_2 \end{aligned}$$

Solving these two equations, i_{e1} and i_{e2} can be calculated.

$$\begin{aligned} i_{e1} &= \frac{(r'_e + R_E) v_1 - R_E v_2}{(r'_e + R_E)^2 - R_E^2} \\ i_{e2} &= \frac{(r'_e + R_E) v_2 - R_E v_1}{(r'_e + R_E)^2 - R_E^2} \end{aligned}$$

The output voltage V_O is given by

D.Suresh, Asst. Prof, ECE Dept, GMRIT

$$\begin{aligned}
 V_O &= V_{C2} - V_{C1} \\
 &= -R_C i_{C2} - (-R_C i_{C1}) \\
 &= R_C (i_{C1} - i_{C2}) \\
 &= R_C (i_{e1} - i_{e2})
 \end{aligned}$$

Substituting i_{e1} , & i_{e2} in the above expression

$$\begin{aligned}
 v_o &= R_C \left\{ \frac{(r_e + R_E)V_1 - R_E V_2}{(r'_e + R_E)^2 - R_E^2} - \frac{(r_e + R_E)V_2 - R_E V_1}{(r'_e + R_E)^2 - R_E^2} \right\} \\
 &= \frac{R_C (v_1 - v_2) (r'_e - 2R_E)}{r'_e (r'_e + 2R_E)} \\
 \text{Therefore, } v_o &= \frac{R_C}{r'_e} (v_1 - v_2) \quad (E-1)
 \end{aligned}$$

Thus a differential amplifier amplifies the difference between two input signals. Defining the difference of input signals as $v_d = v_1 - v_2$ the voltage gain of the dual input balanced output differential amplifier can be given by

$$A_d = \frac{v_o}{v_d} = \frac{R_C}{r'_e}$$

Differential Input Resistance:

Differential input resistance is defined as the equivalent resistance that would be measured at either input terminal with the other terminal grounded. This means that the input resistance R_{i1} seen from the input signal source v_1 is determined with the signal source v_2 set at zero. Similarly, the input signal v_1 is set at zero to determine the input resistance R_{i2} seen from the input signal source v_2 . Resistance R_{S1} and R_{S2} are ignored because they are very small.

$$R_{i1} = \left. \frac{v_1}{i_{b1}} \right|_{v_2 = 0}$$

$$\begin{aligned}
 \text{D.Suresh, Asst. Prof, ECE Dept, GM} \quad &= \left. \frac{v_1}{i_{e1}/\beta} \right|_{v_2 = 0}
 \end{aligned}$$

Substituting i_{e1} ,

$$R_{i1} = \frac{\beta r'_e (r'_e + 2R_E)}{r'_e + R_E}$$

Since $R_E \gg r'_e$
 $\therefore r'_e + 2R_E \gg 2R_E$
 or $r'_e + R_E \gg R_E$
 $\therefore R_{i1} = 2\beta r'_e$ (E-3)

Similarly,

$$R_{i2} = \left. \frac{V_2}{i_{b2}} \right|_{V_1=0}$$

$$= \left. \frac{V_2}{i_{e2} / \beta} \right|_{V_1=0}$$

$$R_{i2} = 2\beta r'_e$$
 (E-4)

The factor of 2 arises because the r'_e of each transistor is in series. To get very high input impedance with differential amplifier is to use Darlington transistors. Another way is to use FET.

Output Resistance:

Output resistance is defined as the equivalent resistance that would be measured at output terminal with respect to ground. Therefore, the output resistance R_{O1} measured between collector C_1 and ground is equal to that of the collector resistance R_C . Similarly the output resistance R_{O2} measured at C_2 with respect to ground is equal to that of the collector resistor R_C .

$$R_{O1} = R_{O2} = R_C \quad (E-5)$$

The current gain of the differential amplifier is undefined. Like CE amplifier the differential amplifier is a small signal amplifier. It is generally used as a voltage amplifier and not as current or power amplifier.