

## Differentiator

As its name implies a **Differentiator** is a circuit that is designed such that the output of the circuit is proportional to the time derivative of the input. The differentiator may be constructed from a basic inverting amplifier if an input resistor is replaced by a capacitor C.

There are two types of differentiator circuits, active and passive.

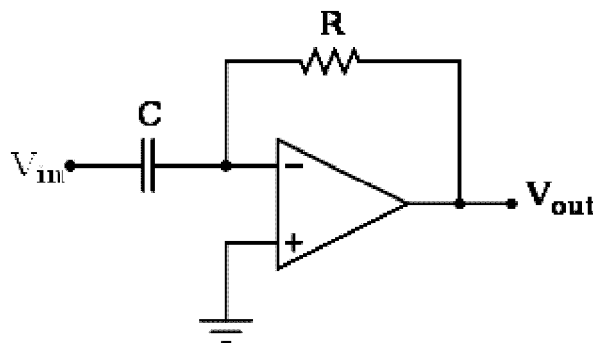


Figure 2.5

A differentiator circuit consists of an operational amplifier, resistors and capacitors. The circuit is based on the capacitors current to voltage relationship:

$$I = C \frac{dV}{dt}$$

where I is the current through the capacitor, C is the capacitance of the capacitor, and V is the voltage across the capacitor. The current flowing through the capacitor is then proportional to the derivative of the voltage across the capacitor. This current can then be connected to a resistor, which has the current to voltage relationship:

$$I = \frac{V}{R}$$

where R is the resistance of the resistor. If V<sub>out</sub> is the voltage across the resistor and V<sub>in</sub> is the voltage across the capacitor, we can rearrange these two equations to obtain the following equation:

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

Thus, it can be shown that in an ideal situation the voltage across the resistor will be proportional to the derivative of the voltage across the capacitor with a gain of RC.

Differentiator circuits are mostly used in signal wave shaping applications, and can be used as a rate –of – change detector in FM modulators.