

CMOS

CMOS:-

MOSFET's are two types

1. N channel mosfet
2. P channel mosfet

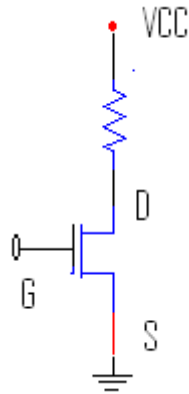


Figure 6.14

It is used as a on off condition switch. If the voltage at gate is more than the source voltage then it is called as on switch

If the gate voltage is less than the source voltage then it simply acts as a off switch

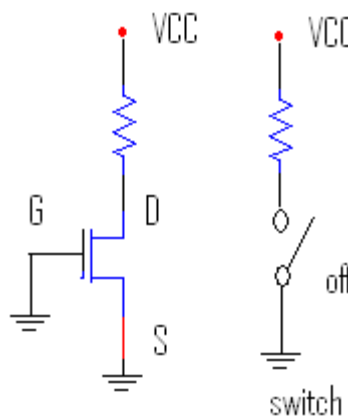


Figure 6.15

CMOS INVERTER

In MOSFET the source and drain can be interchanged. CMOS means complementary metal oxide semi conduction, complementary it contains both P channel MOSFET & N channel

MOSFET, if P channel is in off condition then N channel is in on state & vice versa, P channel MOSFET are called as pull up transistor

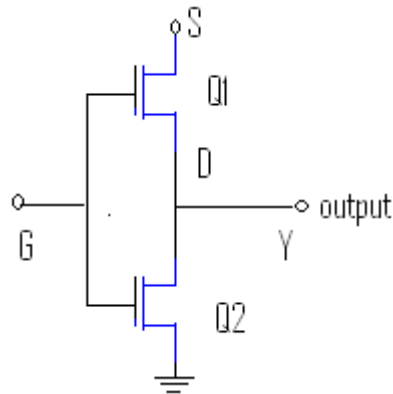


Figure 6.16

V_{CC} is applied to the MOSFET. Bcoz it pulls the output to the high level.

When $A = 1$, Q_1 is OFF, & Q_2 is ON, the output is pulled to low level, the output is directly connected to ground with ON resistance of Q_2 , output, $Y = 0$.

When $A = 0$, Q_1 is ON, & Q_2 is OFF then $Y = 1$ (since output is pulled up to high level through ON resistance)

The ON resistance of any transistor i.e, CMOS transistor is low when logic output is zero when compared to the logic output high (Q_1 is more than Q_2)

CMOS NAND gate:

Q_1 & Q_2 are P channel MOSFETS → pull up transistors

Q_3 & Q_4 are N channel MOSFETS → pull down transistors

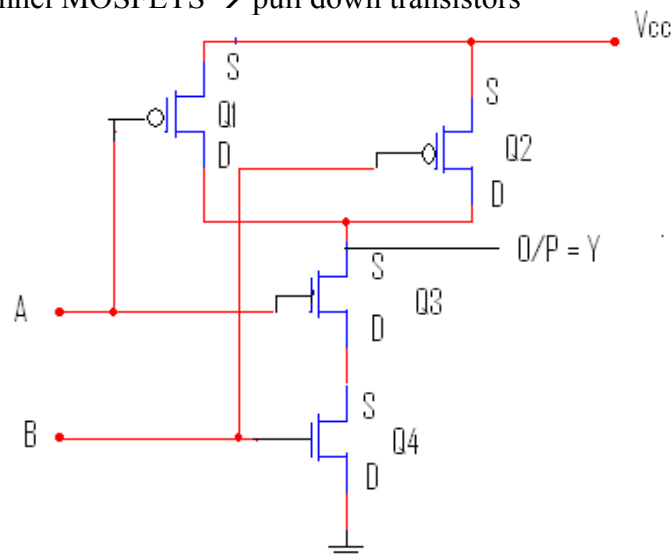


Figure 6.17

A	B	Q ₁	Q ₂	Q ₃	Q ₄	OUTPUT
0	0	ON	ON	OFF	OFF	HIGH
0	1	ON	OFF	OFF	ON	HIGH
1	0	OFF	ON	ON	OFF	HIGH
1	1	OFF	OFF	ON	ON	HIGH

When the both inputs are low the both the transistor Q₁,Q₂ is in ON state & Q₃ & Q₄ is in OFF state then the output is pulled up to high level through the ON resistance of Q₁ & Q₂ in parallel. For the data inputs A = 0 & B = 1 the transistor Q₁,Q₄ is in ON state & Q₂,Q₃ are in OFF state then the output is pulled up to high level through the ON resistance of Q₁.

When the data output's are A = 1 & B = 0 then the transistor Q₂,Q₃ is in ON state & Q₁,Q₄ are in OFF state then the output is pulled up to high level through the ON resistance of Q₂.

For the data A = 1 & B = 1 the transistor Q₁, Q₂ is in OFF state & Q₃, Q₄ are in ON state. Therefore the output is directly connected to ground with the ON resistance of Q₃,Q₄ in series so output is low.